

Inverting Amplifier Questions

Question 1

The equation for the gain of an amplifier is:

- A. $\text{Gain} = V_{\text{out}} \div V_{\text{in}}$
- B. $\text{Gain} = V_{\text{out}} \times V_{\text{in}}$
- C. $\text{Gain} = V_{\text{out}} + V_{\text{in}}$
- D. $\text{Gain} = V_{\text{out}} - V_{\text{in}}$

Question 2

The equation for the gain of an inverting amplifier is:

- A. $\text{Gain} = R_f \div R_i$
- B. $\text{Gain} = - R_f \div R_i$
- C. $\text{Gain} = R_i \div R_f$
- D. $\text{Gain} = - R_i \div R_f$

Question 3

For an inverting amplifier, $R_i = 20 \text{ k}\Omega$ and $R_f = 100 \text{ k}\Omega$. The gain of the amplifier is:

- A. - 100
- B. - 50
- C. - 20
- D. - 5

Question 4

For an inverting amplifier, $R_i = 20 \text{ k}\Omega$ and $R_f = 10 \text{ k}\Omega$. The gain of the amplifier is:

- A. - 20
- B. - 10
- C. - 2
- D. - 0.5

Question 5

For an inverting amplifier, $R_i = 47 \text{ k}\Omega$ and $R_f = 47 \text{ k}\Omega$. The gain of the amplifier is:

- A. - 94
- B. - 47
- C. - 1
- D. zero

Question 6

An inverting amplifier has a gain of -2 . $R_i = 15\text{ k}\Omega$. The value of the feedback resistor is:

- A. $30\text{ k}\Omega$
- B. $17\text{ k}\Omega$
- C. $15\text{ k}\Omega$
- D. $13\text{ k}\Omega$
- E. $7.5\text{ k}\Omega$

Question 7

An inverting amplifier has a gain of -0.1 . $R_i = 68\text{ k}\Omega$. The value of the feedback resistor is:

- A. $68\text{ k}\Omega$
- B. $6.8\text{ k}\Omega$
- C. $680\text{ }\Omega$
- D. $68\text{ }\Omega$

Question 8

An inverting amplifier has a gain of -100 . $R_f = 1\text{ M}\Omega$. The value of the input resistor is:

- A. $1000\text{ k}\Omega$
- B. $100\text{ k}\Omega$
- C. $10\text{ k}\Omega$
- D. $1\text{ k}\Omega$

Question 9

An inverting amplifier has a gain of -0.75 . $R_f = 47\text{ k}\Omega$. The most appropriate value of the input resistor from the E24 series of standard values would be:

- A. $56\text{ k}\Omega$
- B. $62\text{ k}\Omega$
- C. $63\text{ k}\Omega$
- D. $68\text{ k}\Omega$

Question 10

The minimum resistor value of either the input or feedback resistor should be

- A. $1\text{ }\Omega$
- B. $10\text{ }\Omega$
- C. $100\text{ }\Omega$
- D. $1000\text{ }\Omega$

Answers

1. A
2. B
3. D
4. D
5. C
6. A
7. B
8. C
9. B
10. D

Website

http://www.pfnicholls.com/Electronics_Resources/QuestionIndex.html

© Paul Nicholls

August 2022



Electronics Resources by Paul Nicholls is licensed under a [Creative Commons Attribution 4.0 International License](https://creativecommons.org/licenses/by/4.0/).